

SANTIAGO PEÑATE VERA

# PRACTICAL GRID MODELING

This work is licensed under a [Creative Commons](#) “Attribution-ShareAlike 3.0 Unported” license.



# Contents

<i>Introduction</i>	9
<i>General network model</i>	11
<i>Magnitudes and units</i>	13
<i>The branch element</i>	19
<i>The bus and it's connected elements</i>	23
<i>Topology analysis and consolidation</i>	25
<i>Power flow</i>	27
<i>Time series power flow</i>	29
<i>Stochastic power flow</i>	31
<i>State estimation</i>	33
<i>Short-circuit</i>	35

<i>Bibliography</i>	37
---------------------	----

## *List of Figures*

1	Voltage delay.	13
2	Voltage delay in phasor representation in the complex plane.	13
3	Delta connection scheme.	14
4	Wye connection scheme.	14
5	General branch model.	19



## *List of Tables*

1	Electrical magnitudes and their units.	13
2	Magnitudes and their real and imaginary complex components.	13
3	Electrical magnitudes and their per unit base.	15
4	Equations of the generalized $\Pi$ model.	19
5	Three-phase transformer impedances of the branch model.	22





# *Introduction*

This book aims at explaining grid modelling from a practical perspective, providing state of the art models, algorithms as well as implementation hints and examples.

The goal is to provide a reference document for researchers and computer engineers in the field of electric systems modelling, so that the task of building your own simulator or extend the already available open source ones becomes feasible.



*General network model*



# Magnitudes and units

As the electric energy is mostly distributed in altern current, electrical magnitudes are waves that vary their polarity (positive and negative value) and amplitude in time. because of this, the electrical magnitudes are expressed by complex numbers to denote the position of the value in the two-dimensional plane amplitude-time.

The units in electrical grid modelling are represented in the tables 1 and 2.

Magnitude	Unit	Recomended user input unit
Voltage	$V$ (Volt)	$kV$ (kilo-Volt)
Current	$A$ (Ampere)	$kA$ (kilo-Ampere)
Potencia	$VA$ (Volt-Ampere)	$MVA$ (Mega-Volt-Ampere)
Active power	$W$ (Watt)	$MW$ (Mega-Watt)
Reactive power	$VAr$ (Volt-Ampere-reactive)	$MVAr$ (Mega-Volt-Ampere-reactive)
Impedance	$\Omega$ (Ohm)	$\Omega$ (Ohm) or per-unit
Admittance	$S$ (Siemens)	$S$ (Siemens) or per-unit

The figure 1 shows two voltage waves. The one represented with a dotted line is delayed an angle  $\delta$  with respect to the reference voltage wave represented by the plain black line. Since both waves are periodical, both can be represented as "phasors" or vectors indicating the magnitude's value and angle in the complex rectangular plane as depicted in the figure 2. Figures 1 and 2 are equivalent representations.

Magnitude	Real part	Imaginary part	Relation
$S$ (Power)	$P$ (Active power)	$Q$ (Reactive power)	$S = P + jQ$
$V$ (Voltage)	$V_r$ (Real voltage)	$V_i$ (Imaginary voltage)	$V = V_r + jV_i$
Expressed as	$V_m$ (Voltage module) $\delta$ (Voltage angle)		$V = V_m \cdot e^{j\delta}$
$I$ (Current)	$I_r$ (Real current)	$I_i$ (Imaginary current)	$I = I_r + jI_i$
$Z$ (Impedance)	$R$ (Resistance)	$X$ (Inductance)	$Z = R + jX$
$Y$ (Admittance)	$G$ (Conductance)	$B$ (Susceptance)	$Y = G + jB$

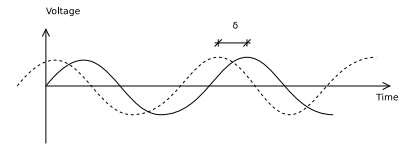


Figure 1: Voltage delay.

Table 1: Electrical magnitudes and their units.

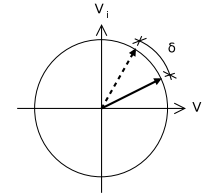


Figure 2: Voltage delay in phasor representation in the complex plane.

Table 2: Magnitudes and their real and imaginary complex components.

### Components connection and their conversions

Let us assume a three-phase grid. The phases of the grid are denoted by the names of A, B and C. There are two main connection types that arise: Wye (like the letter "y") and Delta.

The wye and delta connections provide the ground to introduce the *phase* and *line* voltages. The phase to neutral voltage is called *phase voltage*, those are  $V_A$ ,  $V_B$  and  $V_C$ . The phase to phase voltage is called *line voltage*, those are  $V_{AB}$ ,  $V_{AC}$  and  $V_{BC}$ .

The *delta connection* is depicted in the figure 3. The delta connection has no neutral.

The *wye connection* is depicted in the figure 4. The star connection does have neutral (N). The wye connection is also known as star connection.

*Delta to Wye ( $\Delta \rightarrow Y$ )* The transformation of a three phase connected shunt element in Delta to it's Wye equivalent is:

$$Elm_{Wye} = D \times Elm_{Delta} \quad (1)$$

Where  $D$  is:

$$D = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix} \quad (2)$$

For instance, considering the impedances transformation from figures 3 and 4:

$$\begin{bmatrix} Z_A \\ Z_B \\ Z_C \end{bmatrix} = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix} \times \begin{bmatrix} Z_{AB} \\ Z_{AC} \\ Z_{BC} \end{bmatrix} \quad (3)$$

*Wye to Delta ( $Y \rightarrow \Delta$ )* The transformation of a three phase connected shunt element in Wye to it's Delta equivalent is:

$$Elm_{Delta} = D^{-1} \times Elm_{Wye} \quad (4)$$

Where  $D^{-1}$  is:

$$D^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 0 & -1 \\ -1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \quad (5)$$

For instance, considering the impedances transformation from figures 3 and 4:

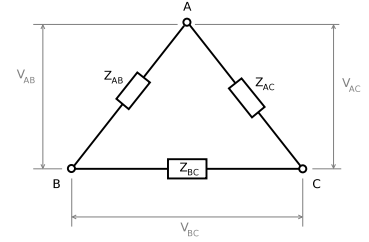


Figure 3: Delta connection scheme.

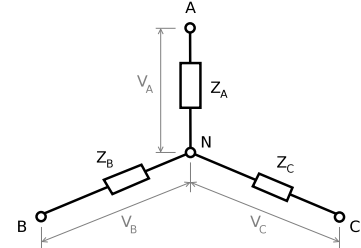


Figure 4: Wye connection scheme.

$$\begin{bmatrix} Z_{AB} \\ Z_{AC} \\ Z_{BC} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 0 & -1 \\ -1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \times \begin{bmatrix} Z_A \\ Z_B \\ Z_C \end{bmatrix} \quad (6)$$

### Per unit system

In an electrical grid there are multiple levels of voltage. This situation introduces discontinuities in the numerical methods used to solve power flows and state estimations among others, producing an unstable convergence behaviour. To avoid this, the per unit system is introduced. A side effect of the per unit representation is to have a very convenient way of visualizing the grid magnitudes, all referenced to their base. In the per unit system, all the voltages are expressed in terms of their nominal value. In this case, all the grid voltage values are around one. For instance, a voltage value of 0.98 means that the voltage is 98 % of the nominal voltage value at that point.

For most exchange formats in computer programs, the element's magnitudes are expressed with a mix of actual units and per unit values. Regardless of this, a practical way of converting any electrical magnitude to its per unit equivalent is presented.

First, we must choose an arbitrary value of power base conversion. This value can be seen as the grid's nominal power, even though that concept is not related to any physical quantity, but it is rather a numerical artifice.

The base power is most commonly chosen to be  $S_{Base} = 100\text{MVA}$ .

Magnitude	Base
$V$ (Voltage)	$V_{Base}$ : terminal's nominal voltage.
$S$ (Power)	$S_{Base}$ : Arbitrary value.
$I$ (Current)	$I_{Base} = S_{Base} / V_{line_{Base}} = S_{Base} / (V_{Base} \cdot \sqrt{3})$
$Z$ (Impedance)	$Z_{Base} = S_{Base} / V_{Base}^2$
$Y$ (Admittance)	$Y_{Base} = 1 / Z_{Base}$

Table 3: Electrical magnitudes and their per unit base.

### Sequence components simplification

Charles L. Fortescue presented in 1918 his famous article <sup>1</sup> in which he describes how to represent a three-phase element in the so-called *sequence components*.

The main use of this technique is to reduce the amount of impedances needed to represent a line or transformer from usually nine, to three (or even two) if the element is considered to be balanced. An element is considered balance if the impedance in all it's phases is equal and

<sup>1</sup> Charles L Fortescue. Method of symmetrical co-ordinates applied to the solution of polyphase networks. *Transactions of the American Institute of Electrical Engineers*, 37(2):1027–1140, 1918

the phase-to-phase coupling impedances are also equal. This is an assumption that is commonly made for transmission grids (very high voltage) and distribution grids in high voltage. This advance allowed the popularization of the single-line diagrams in which every line represents a number of wires transmitting power in a balanced scheme.

Fortescue defined a transformation matrix  $A_s$  and its inverse as:

$$A_s = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \quad (7)$$

$$A_s^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \quad (8)$$

Where  $a$  is the transformation eigenvector:

$$a = 1^{120_{deg}} = 1 \cdot e^{j\frac{2}{3}\pi} = 1 \cdot \cos\left(\frac{2}{3}\pi\right) + 1j \cdot \sin\left(\frac{2}{3}\pi\right) \quad (9)$$

$$a^2 = 1^{-120_{deg}} = 1 \cdot e^{-j\frac{2}{3}\pi} = 1 \cdot \cos\left(\frac{2}{3}\pi\right) - 1j \cdot \sin\left(\frac{2}{3}\pi\right) \quad (10)$$

Then, any 3x3 impedance matrix representing the rectangular ABC three-phase impedance of an element (line, transformer, capacitor, etc.) can be transformed to a sequence equivalent using the formula:

$$Z_{seq} = A_s^{-1} \times Z_{ABC} \times A_s \quad (11)$$

*Example* Consider the following impedance matrix of a three-phase line. Example from <sup>2</sup>.

<sup>2</sup> William H Kersting. *Distribution system modeling and analysis*. CRC press, 2012

$$Z_{ABC} = \begin{bmatrix} 0.4576 + j1.0780 & 0.1560 + j0.5017 & 0.1535 + j0.3849 \\ 0.1560 + j0.5017 & 0.4666 + j1.0482 & 0.1580 + j0.4236 \\ 0.1535 + j0.3849 & 0.1580 + j0.4236 & 0.4615 + j1.0651 \end{bmatrix}$$

Using equation 11, we obtain the sequence impedance matrix:

$$Z_{seq} = \begin{bmatrix} 0.7735 + j1.9373 & 0.0256 + j0.0115 & 0.0321 + j0.0159 \\ -0.0321 + j0.0159 & 0.3061 + j0.6270 & 0.0723j0.0060 \\ 0.0256 + j0.0115 & -0.0723j0.0059 & 0.3061 + j0.6270 \end{bmatrix}$$

For the sequence matrix, the non diagonal elements are neglected. Using only the three diagonal elements as:

$$Z_0 = 0.7735 + j1.9373$$

$$Z_1 = 0.3061 + j0.6270$$

$$Z_2 = 0.3061 + j0.6270$$



Observe that  $Z_1$  and  $Z_2$  are identical (with the shown numerical precision). It is very common in utilities to store only  $Z_0$  and  $Z_1$  to define a line. The balanced element assumption is very common and should be carefully used.

### *Bulding $Z_{ABC}$ from the sequence components*

Once the complete 3x3 impedance matrix has been reduced to the sequence components and only those have been stored in the utility database, the obtaining of the full 3x3 matrix might be necessary to perform unbalanced calculations. Of course we will not be able to obtain the exact original  $Z_{ABC}$  from the reduced sequence components, but the approximation is fair.

The approximated full impedance matrix is obtained from the sequence components as:

$$Z_{ABC_{approx}} = \frac{1}{3} \begin{bmatrix} 2Z_1 + Z_0 & Z_0 - Z_1 & Z_0 - Z_1 \\ Z_0 - Z_1 & 2Z_1 + Z_0 & Z_0 - Z_1 \\ Z_0 - Z_1 & Z_0 - Z_1 & 2Z_1 + Z_0 \end{bmatrix} \quad (12)$$

*Example* We need to compute two values, before assambling the 3x3 matrix:

$$\frac{1}{3}(2 \cdot Z_1 + Z_0) = \frac{1}{3}(2 \cdot (0.3061 + j0.6270) + (0.7735 + j1.9373)) = 0.4619 + j1.0638$$

$$\frac{1}{3}(Z_0 - Z_1) = \frac{1}{3}((0.7735 + j1.9373) - (0.3061 + j0.6270)) = 0.1558 + j0.4368$$

The the approximated impedance matrix is:

$$Z_{ABC_{approx}} = \begin{bmatrix} 0.4619 + j1.0638 & 0.1558 + j0.4368 & 0.1558 + j0.4368 \\ 0.1558 + j0.4368 & 0.4619 + j1.0638 & 0.1558 + j0.4368 \\ 0.1558 + j0.4368 & 0.1558 + j0.4368 & 0.4619 + j1.0638 \end{bmatrix}$$

We observe that the calculation outcome is a fair approximation of the original  $Z_{ABC}$  and that the approximated matrix is symmetric, matching the balanced assumption, which the original impedance matrix did not fully comply with. Therefore, is the original  $Z_{ABC}$  was reduced assuming a balanced impedance distribution when that was not the case, if we build the approximated matrix, we will never know if it represents the reality.



## The branch element

To the effect of most calculations run in operation of a electrical system, the lines, transformers, and any other element that connects two nodes are represented by the so-called  $\Pi$  model.

### $\Pi$ Model

The pi model is composed by a series admittance and a shunt admittance divided in two, connected at the sending and receiving terminals (primary and secondary). To accomodate the transformers and voltage regulators and the possibility of at the sending and/or receiving terminals, two per-unit transformers are included as well.

The series admittance  $Y_{series}$  is computed as the inverse of  $Z_{ABC}$ . From the line's calculation it is obtained the series impedance matrix  $Z_{ABC}$  and the shunt admittance matrix  $Y_{sh}$ .

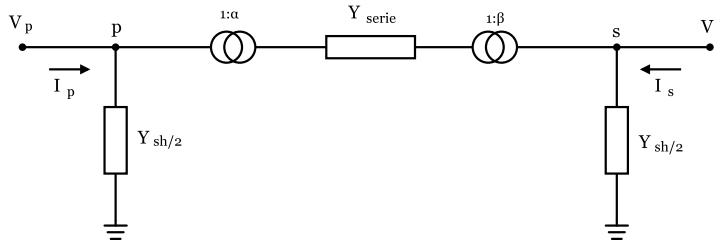


Figure 5: General branch model.

The generalized admittance matrix that corresponds to the  $\Pi$  model is:

$$\begin{bmatrix} I_p \\ I_s \end{bmatrix} = \begin{bmatrix} Y_{pp} & Y_{ps} \\ Y_{sp} & Y_{ss} \end{bmatrix} \times \begin{bmatrix} V_p \\ V_s \end{bmatrix} \quad (13)$$

Where:

$Y_{pp}$	$Y_{ps}$	$Y_{sp}$	$Y_{ss}$
$\frac{Y_{series} + \frac{Y_{sh}}{2}}{\alpha^2}$	$\frac{-Y_{series}}{\alpha\beta}$	$\frac{-Y_{series}}{\alpha\beta}$	$\frac{Y_{series} + \frac{Y_{sh}}{2}}{\beta^2}$

Table 4: Equations of the generalized  $\Pi$  model.

The formula 13 will be used to compute the network admittance matrices.

### Line

The line element, utilizes the branch model as it has been formulated, only that the use of the tap ratio relations  $\alpha$  and  $\beta$  is not necessary.

*Example* Let's assume that we have already computed the series impedance and the shunt admittance of a three-phase line. The nominal voltage at the line terminals is  $66kV$  and we choose the base power to be  $S_{base} = 100MVA$ .

$$Z_{ABC} = \begin{bmatrix} 0.4576 + j1.0780 & 0.1560 + j0.5017 & 0.1535 + j0.3849 \\ 0.1560 + j0.5017 & 0.4666 + j1.0482 & 0.1580 + j0.4236 \\ 0.1535 + j0.3849 & 0.1580 + j0.4236 & 0.4615 + j1.0651 \end{bmatrix} \Omega$$

$$Y_{sh} = \begin{bmatrix} j5.6712 & -j1.8362 & -j0.7034 \\ -j1.8362 & j5.9774 & -j1.1690 \\ -j0.7034 & -j1.1690 & j5.3911 \end{bmatrix} \cdot 10^{-6} S$$

The first thing we need to do is to compute the base magnitudes:

$$Z_{base} = \frac{100MVA}{(66kV)^2} = 0.022956841 \quad \Omega$$

$$Y_{base} = \frac{1}{Z_{base}} = 43.56 \quad S$$

Then we must obtain the line series admittance matrix  $Y_{series}$  by inverting the  $3 \times 3$  matrix  $Z_{ABC}$ . Then we divide the resulting matrix by  $Y_{base}$ . Analogously we can invert the per unit impedance matrix:

$$Y_{series} = \left( \frac{Z_{ABC}}{Z_{base}} \right)^{-1} \quad p.u.$$

$$Y_{series} = \begin{bmatrix} 0.0112 - j0.0232 & -0.0054 + j0.008 & -0.0020 + j0.0052 \\ -0.0054 + j0.008 & 0.0125 - j0.024 & -0.0033 + j0.0063 \\ -0.0020 + j0.0052 & -0.0033 + j0.0063 & 0.0100 - j0.0224 \end{bmatrix} \quad p.u.$$

Dividing the shunt admittance by the base admittance we obtain the per unit shunt admittance:

$$Y_{sh} = \begin{bmatrix} j13.0193 & -j4.2153 & -j1.6148 \\ -j4.2153 & j13.7222 & -j2.6837 \\ -j1.6148 & -j2.6837 & j12.3763 \end{bmatrix} \cdot 10^{-8} \quad p.u.$$

Now we need to find the branch model admittances  $Y_{pp}$ ,  $Y_{ps}$ ,  $Y_{sp}$  and  $Y_{ss}$ .

$$Y_{pp} = Y_{ss} = Y_{series} + Y_{sh}/2 = \begin{bmatrix} 0.0112 - j0.0232 & -0.0054 + j0.008 & -0.0020 + j0.0052 \\ -0.0054 + j0.008 & 0.0125 - j0.024 & -0.0033 + j0.0063 \\ -0.0020 + j0.0052 & -0.0033 + j0.0063 & 0.0100 - j0.0224 \end{bmatrix} \quad p.u.$$

$$Y_{ps} = Y_{sp} = -Y_{series} = \begin{bmatrix} -0.0112 + j0.0232 & 0.0054 - j0.008 & 0.0020 - j0.0052 \\ 0.0054 - j0.008 & -0.0125 + j0.024 & 0.0033 - j0.0063 \\ 0.0020 - j0.0052 & 0.0033 - j0.0063 & -0.0100 + j0.0224 \end{bmatrix} \quad p.u.$$

If we convert the three-phase matrices into positive sequence values we obtain:

$$Y_{pp} = Y_{ss} = 0.0148 - j0.0296$$

$$Y_{ps} = Y_{sp} = -0.0148 + j0.0296$$

$$\begin{bmatrix} I_p \\ I_s \end{bmatrix} = \begin{bmatrix} 0.0148 - j0.0296 & -0.0148 + j0.0296 \\ -0.0148 + j0.0296 & 0.0148 - j0.0296 \end{bmatrix} \times \begin{bmatrix} V_p \\ V_s \end{bmatrix}$$

### Transformer

The transformer model implements the branch model as well, but the model admittances  $Y_{pp}$ ,  $Y_{ps}$ ,  $Y_{sp}$  and  $Y_{ss}$  vary depending on the connections of the transformer at the primary and at the secondary.

The most common transformer connections at the terminals are:

- Delta ( $\Delta$ )
- Wye ( $Y$ )
- Grounded Wye (the neutral is grounded) ( $Yg$ )

The table 5 lays out the branch admittances for every pair of connections. The source for this model is the excellent book by J.Arrillaga<sup>3</sup>.

<sup>3</sup> Jos Arrillaga and CP Arnold. *Computer analysis of power systems*. Wiley Online Library, 1990

$$Y_I = \begin{bmatrix} y_t & 0 & 0 \\ 0 & y_t & 0 \\ 0 & 0 & y_t \end{bmatrix} \quad (14)$$

$$Y_{II} = \begin{bmatrix} 2y_t & -y_t & -y_t \\ -y_t & 2y_t & -y_t \\ -y_t & -y_t & 2y_t \end{bmatrix} \quad (15)$$

Primary	Secondary	$Y_{pp}$	$Y_{ss}$	$Y_{ps}$ and $Y_{sp}$
$Yg$	$Yg$	$\frac{1}{\alpha^2} Y_I$	$\frac{1}{\beta^2} Y_I$	$-\frac{1}{\alpha\beta} Y_I$
$Yg$	$Y$	$\frac{1}{3\alpha^2} Y_{II}$	$\frac{1}{3\beta^2} Y_{II}$	$-\frac{1}{3\alpha\beta} Y_{II}$
$Yg$	$\Delta$	$\frac{1}{\alpha^2} Y_I$	$\frac{1}{\beta^2} Y_{II}$	$\frac{1}{\alpha\beta} Y_{III}$
$Y$	$Yg$	$\frac{1}{3\alpha^2} Y_{II}$	$\frac{1}{3\beta^2} Y_{II}$	$-\frac{1}{3\alpha\beta} Y_{II}$
$Y$	$Y$	$\frac{1}{3\alpha^2} Y_{II}$	$\frac{1}{\beta^2} Y_{II}$	$\frac{1}{\alpha\beta} Y_{III}$
$\Delta$	$\Delta$	$\frac{1}{\alpha^2} Y_{II}$	$\frac{1}{\beta^2} Y_{II}$	$-\frac{1}{\alpha\beta} Y_{II}$
$\Delta$	$Yg$	$\frac{1}{\alpha^2} Y_{II}$	$\frac{1}{\beta^2} Y_I$	$\frac{1}{\alpha\beta} Y_{III}$

Table 5: Three-phase transformer impedances of the branch model.

$$Y_{III} = \begin{bmatrix} -y_t & y_t & 0 \\ 0 & -y_t & y_t \\ y_t & 0 & -y_t \end{bmatrix} \quad (16)$$

$y_t$  is the transformer winding per unit admittance. It is given in values per units from the transformer especifications sheet. Usually it is given either directly as leakage resistance  $r_l$  and inductance  $x_l$ , in which case:

$$y_t = \frac{1}{r_l + jx_l} \quad (17)$$

Or it is given as the "short circuit study" values. This is a more complete case.

### *Voltage regulator*

Since all the electrical models are in per-unit values, the voltage regulator is modeled exactly the same as a transformer.

# *The bus and it's connected elements*

*The substation*

*Types of buses*

*Load*

*Voltage controlled generator*

*Battery*

*Capacitor banks*





# *Topology analysis and consolidation*

*Islands detection*

*Calculation of the bus connected phases*

*Calculation of the admittance matrices*

*Calculation of the voltage, power and current vectors*



# *Power flow*

*Z-Matrix*

*Newton-Raphson*

*Levenberg-Marquardt*

*Holomorphic embedding*



*Time series power flow*



# *Stochastic power flow*

*Cumulative Density Function (CDF)*

*Monte Carlo*

*Latin Hypercube*





*State estimation*



*Short-circuit*



## *Bibliography*

Jos Arrillaga and CP Arnold. *Computer analysis of power systems*. Wiley Online Library, 1990.

Charles L Fortescue. Method of symmetrical co-ordinates applied to the solution of polyphase networks. *Transactions of the American Institute of Electrical Engineers*, 37(2):1027–1140, 1918.

William H Kersting. *Distribution system modeling and analysis*. CRC press, 2012.